

Digital Design

RTL Design

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

<http://jatinga.iitg.ac.in/~asahu/cs221/>


Announcement

- **Quiz on Friday : 8AM to 9AM**
- **Syllabus : topic covered upto 22nd Oct Lecture**
 - Basic latch, FF, reg, ctr, mem
 - FSM based design and Implementation, FSM completeness and Correctness
 - FSM Optimization: RM and Partitioning method
- **Venue : 4201, 4202, 4204, 4205**

Outline

- Simple ASM Examples
- Data Path : R2, R2 and R3
- CP+DP: Mod 14 counter
- Classic Example : Sequential Multiplier
- Verilog Code for Multiplier
- FPGA: Introduction

ASM charts : 3 Elements used

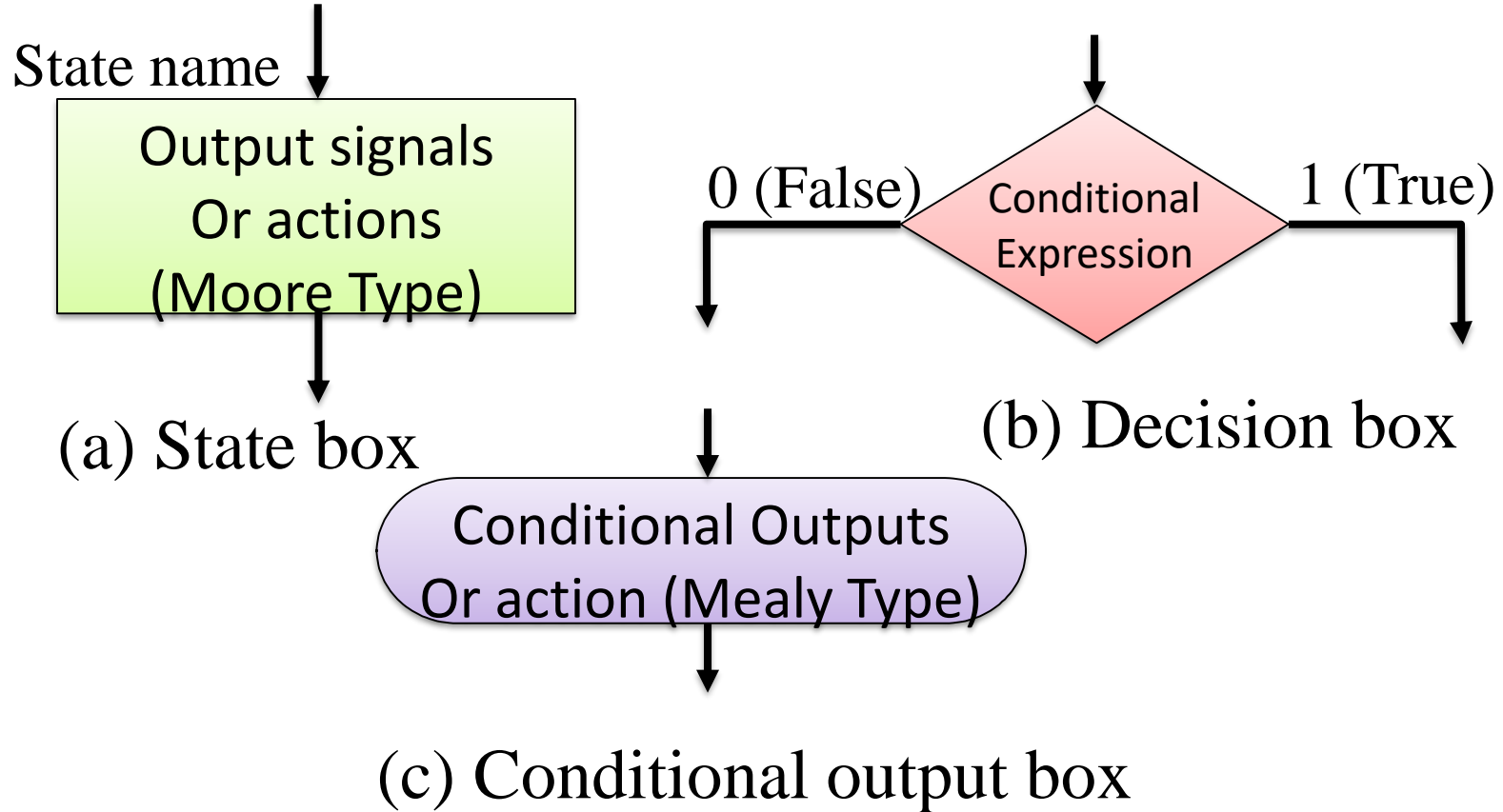


Another Example: Ex 9

ASM Design Example

- Find the ASM chart corresponding to the following description
 - There are two states A, B
 - If in state A and input X is `0' then the next state is A
 - If in state A and input X is `1' then the next state is B
 - If in state B and input Y is `1' then the next state is B
 - If in state B and input Y is `0' then the next state is A
 - Output Z is equal to `1' while the circuit is in state B
- Solution:
 - Total States $\rightarrow 2$
 - Two Inputs $\rightarrow X, Y$
 - One Output $\rightarrow Z$


ASM Design Example

 

Another Example : Ex 10


Another Example: From FSM to ASM

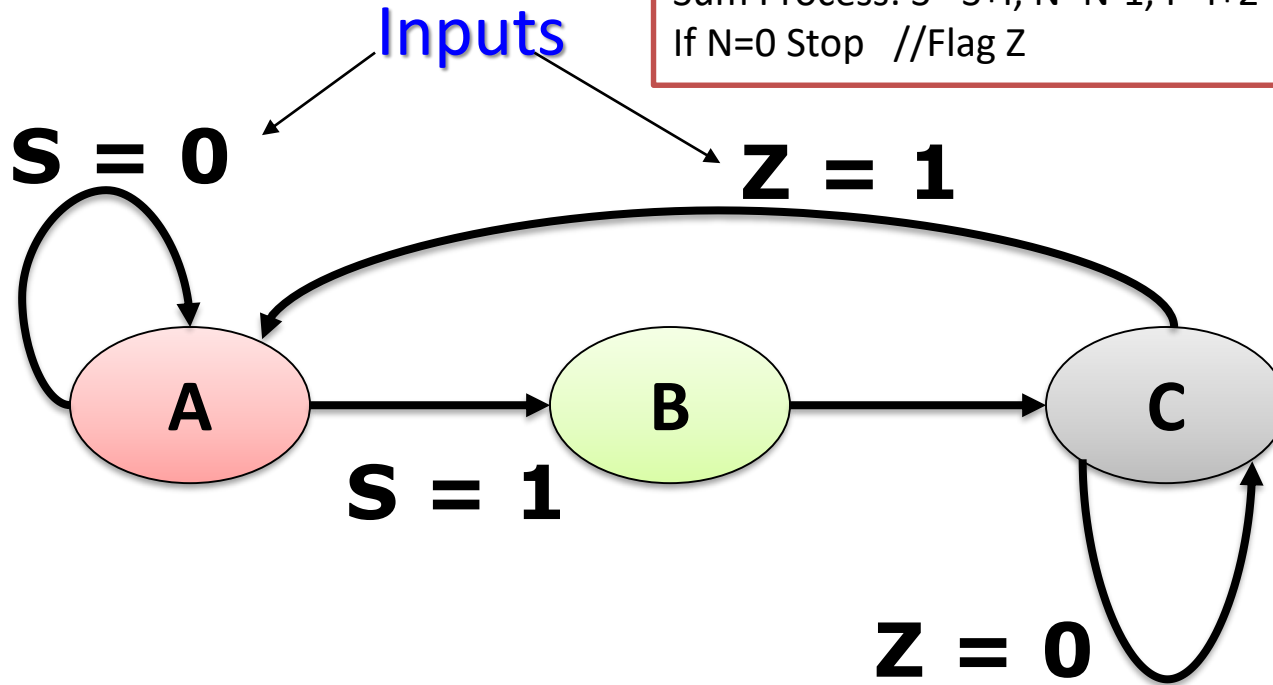If $S = 1$, Start the Sum Process, initialize N , $I = 1$
Sum Process: $S = S + I$, $N = N - 1$, $I = I + 2$
If $N = 0$ Stop //Flag Z




Similar to the ASM of : Sum of First N odd numbers

Another Example: From FSM to ASM

 

 
If $S = 1$, Start the Sum Process,
initialize N
Sum Process: $S = S + 1$, $N = N - 1$
If $N = 0$ Stop //Flag Z



ASM Block


ASM Blocks

One ASM block
execute in one cycle

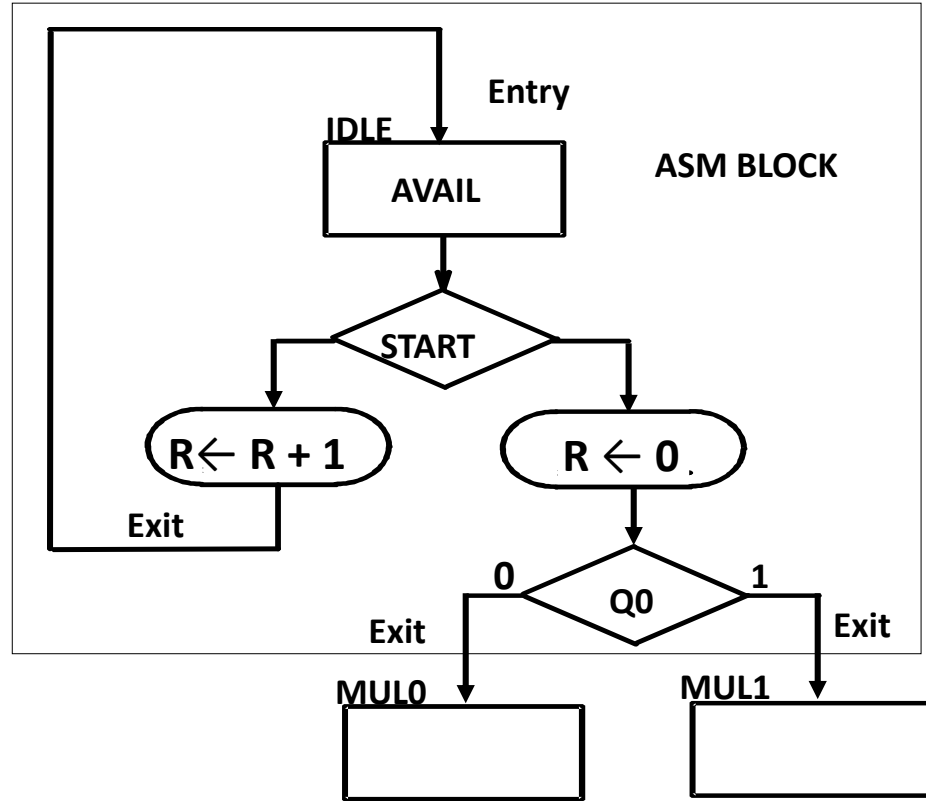

ASM Timing

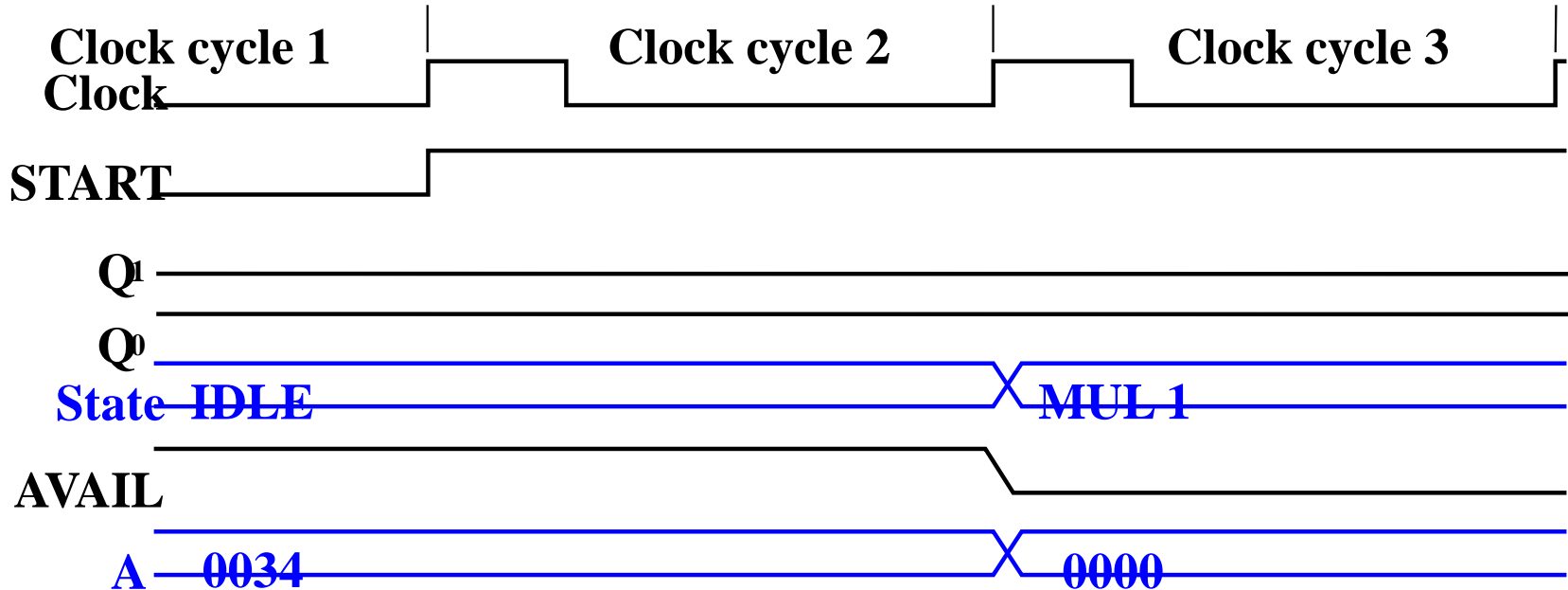- Outputs appear while in the state
- Register transfers occur at the clock while exiting the state - New value occur in the next state!



Another Example : Ex 11

ASM : DP+CP Example

- Find the Data Path and ASM for the following problem:
 - We **first** need to load two registers (R1, R2) with some value.
 - We will **then** need to add the two Registers (R1, R2) and save the result in Register R3.
 - All these operations **should occur if** a “**start**” Signal is activated.


ASM : DP+CP Example

- Translation to Hardware:
 - We need to clear the registers first.
 - If the “**start**” signal is set to 0, I do nothing
 - Else If the “**start**” signal is set to 1, I will load R1, R2 with values
 - Next, enable R3 to be loaded (load-2) by the results of $R1+R2$


ASM : DP+CP Example

- Inputs/Outputs:
 - **start** is an input signal (Use a switch)
 - **clear** is an output signal generated and connected to R1, R2, R3
 - **load-1** is an output signal generated and connected to R1, R2
 - **load-2** is an output signal generated and connected to R3

Data Path

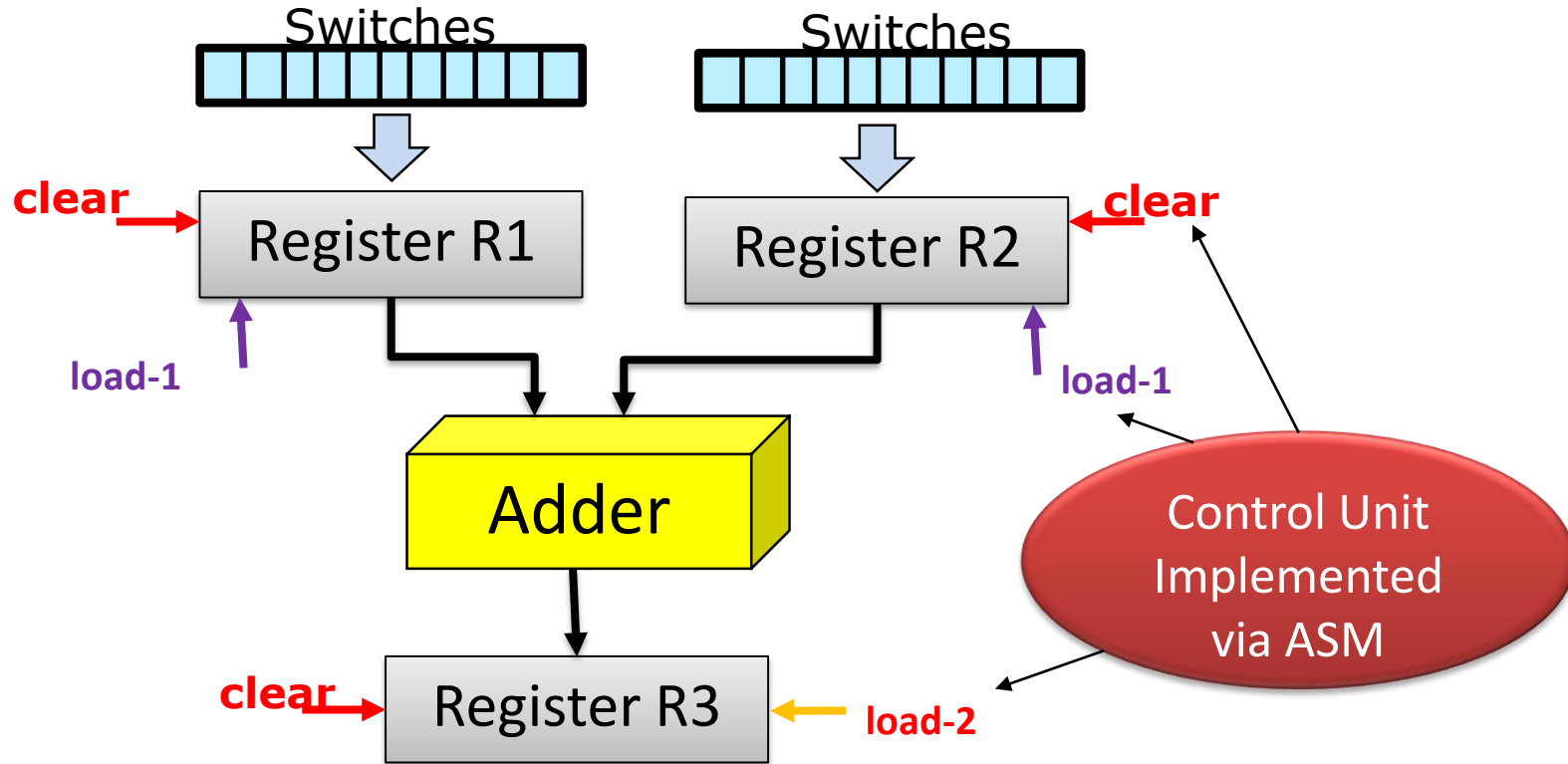

ASM : DP+CP Example

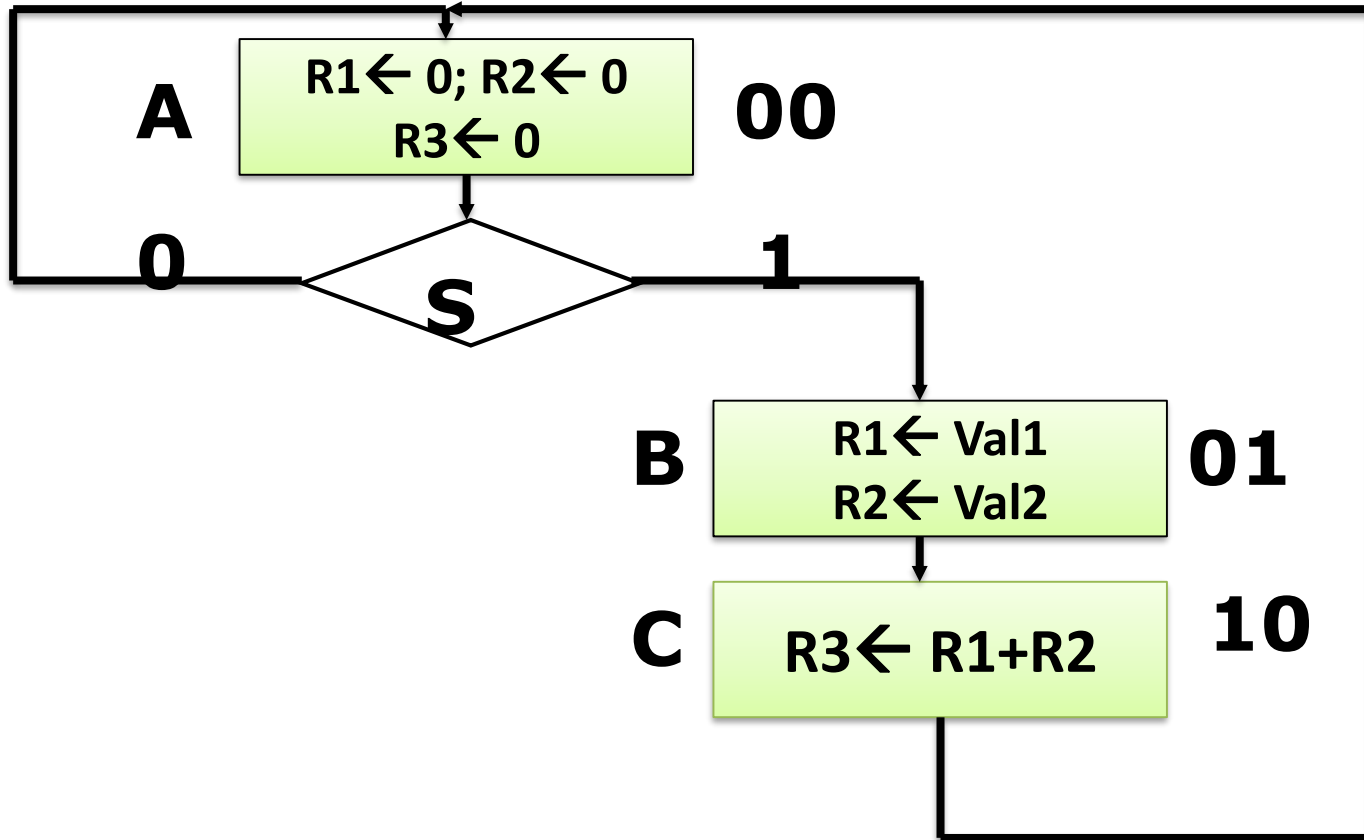

ASM : DP+CP Example Controller


PS		S	NS	
0	0	0	0	0
0	0	1	0	1
0	1	X	1	0
1	0	X	0	0
1	1	X	0	0

PS		CLR	L1	L2
0	0	1	0	0
0	1	0	1	0
1	0	0	0	1
1	1	X	X	X

$$D1 = Q1'.Q0 \quad D2 = S.Q1'.Q0'$$

$$CLR = Q1'.Q0' \quad L1 = Q0'.Q1 \quad L2 = Q1.Q0'$$

Data Path

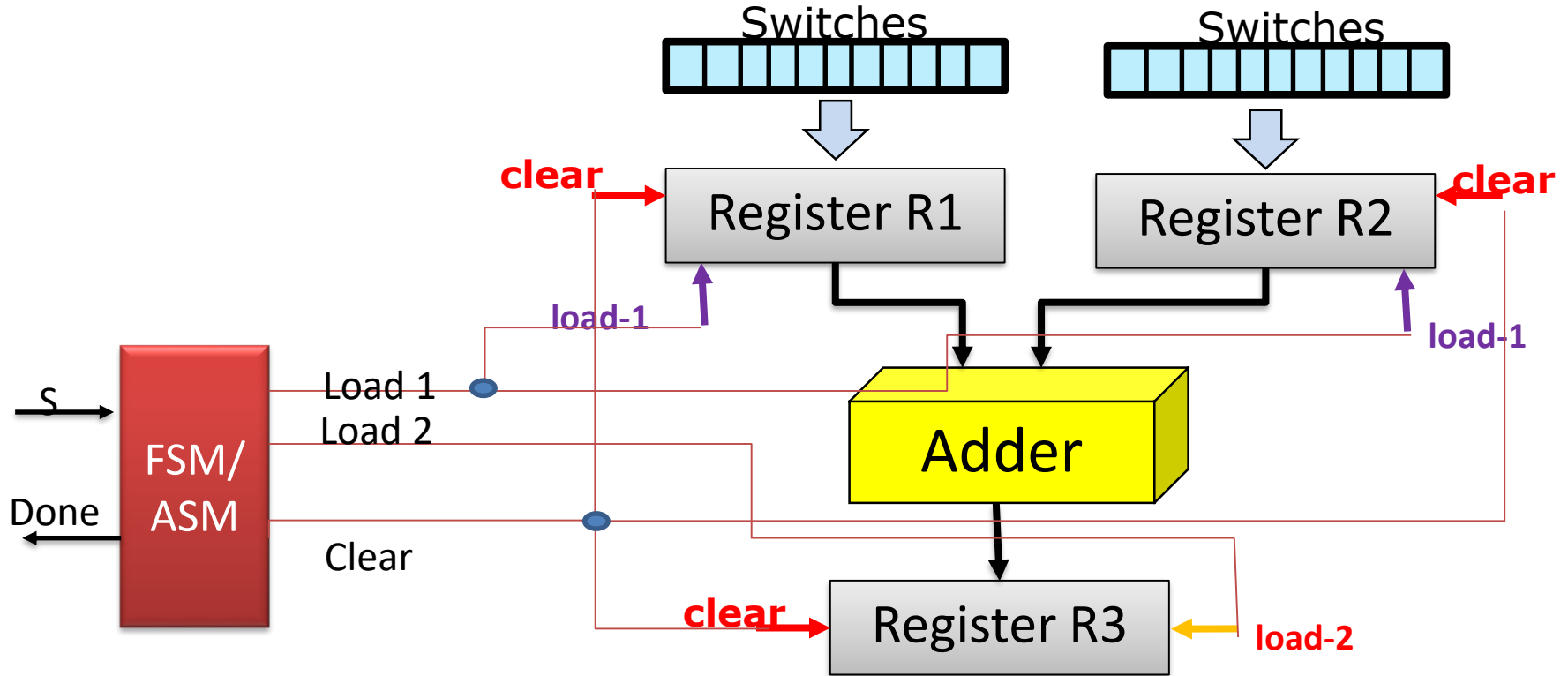

ASM Charts: An Complete Example

Ref: Mano Book

Ex 12: The Dozenth One

ASM Charts: An Example


Mod 14 counter:

- There is a 4 bit counter (A)
- E specify: less than 12_{10} or less than 4_{10}
- EF=11 specify : value = 12_{10} ,
 - **It time to reset after next counting**
- E depends of A_2 , F depends on A_3 and A_2

If $A_2=1 \rightarrow E=1$, else $E=0$

$A_3A_2=1, \rightarrow F=1$, counter reset

AMS DP+CP : to be High Level

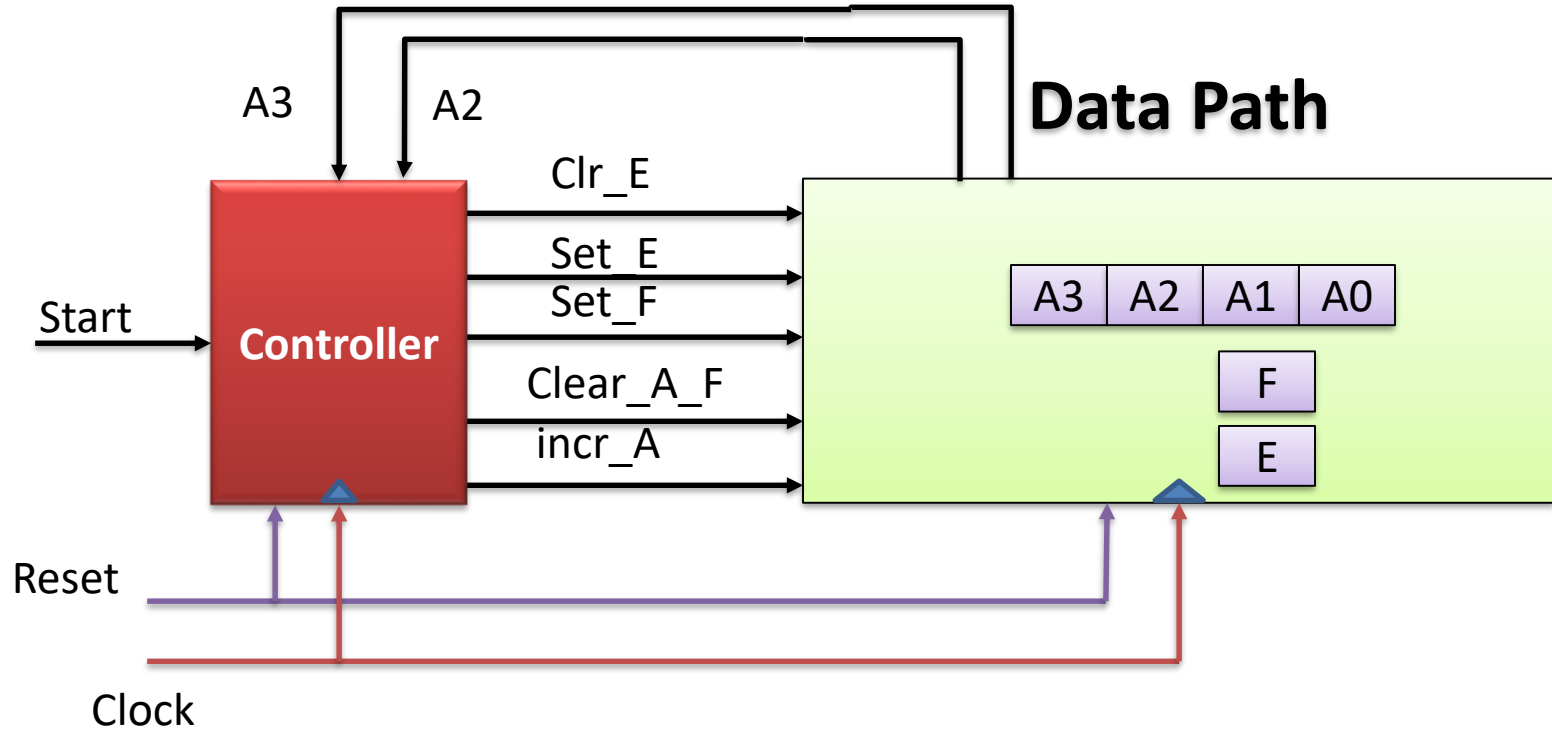


ASM Charts: An Example

- A is a register;
- A_i stands for i^{th} bit of the A register.

$$A = A_3A_2A_1A_0$$


- E and F are single-bit flip-flops.

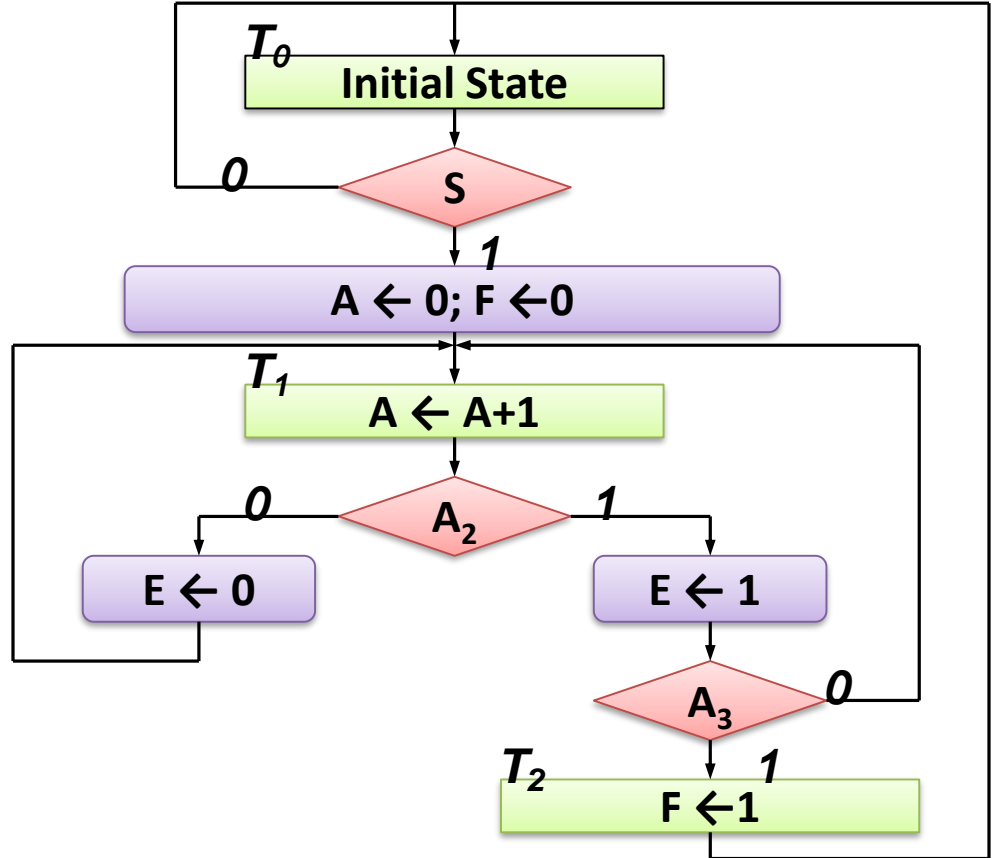

Timing in ASM Charts

- Operations of ASM can be illustrated through a timing diagram.
- Two factors which must be considered are
 - Operations in an **ASM block** occur at the same time in *one clock cycle*
 - Decision boxes are dependent on the status of the *previous clock cycle* (that is, they do not depend on operations of current block)

Timing in ASM Charts

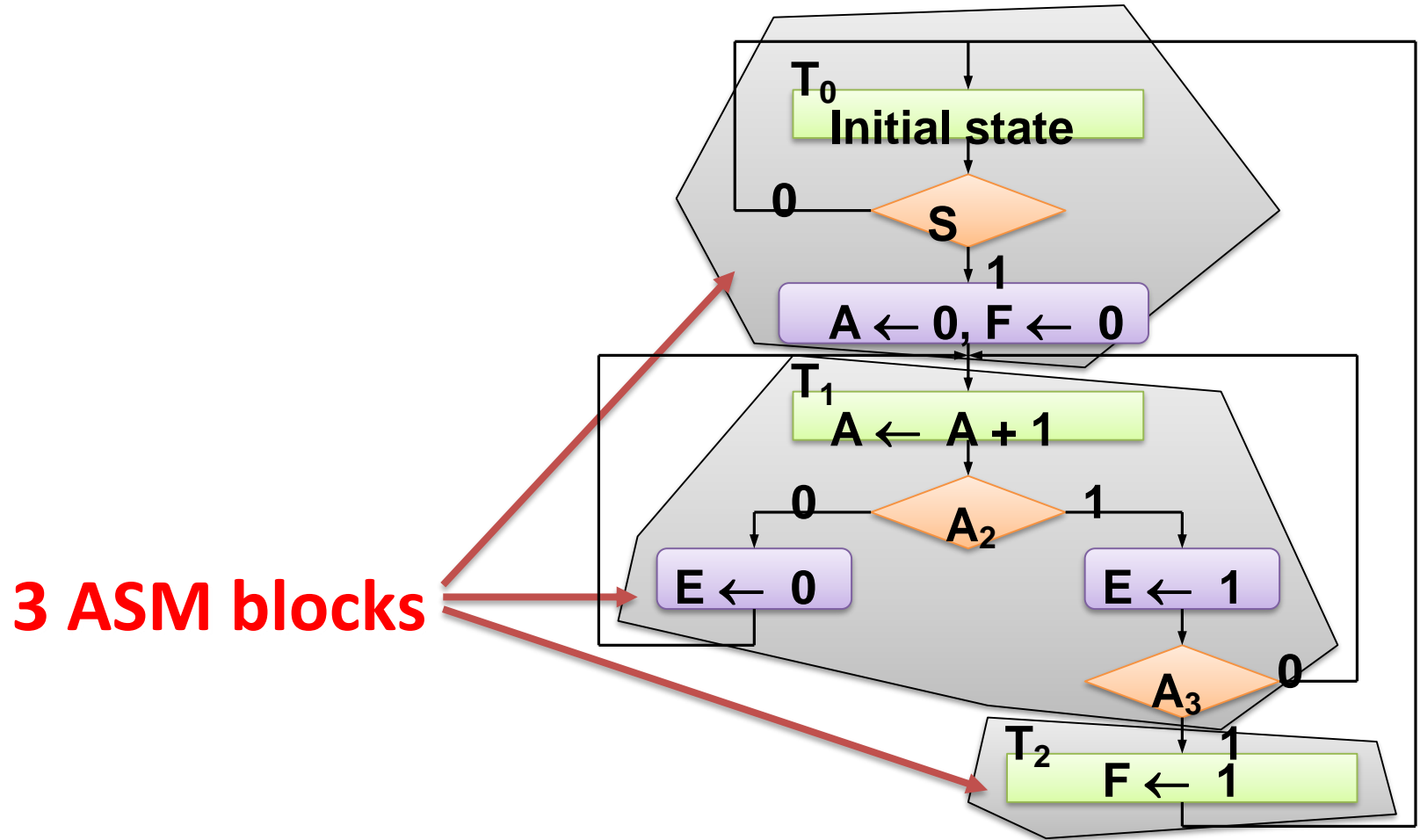


Timing in ASM Charts

- Operations of ASM can be illustrated through a timing diagram.
- Two factors which must be considered are
 - Operations in an ASM block occur at the same time in *one clock cycle*
 - Decision boxes are dependent on the status of the *previous clock cycle* (that is, they do not depend on operations of current block)

Timing in ASM Charts

CTR	E, F	Conditions	State
0000	1,0	$A_2=0, A_3=0$	T1
0001	0,0	--	--
0010	0,0	---	--
0011	0,0	---	--
0100	0,0	$A_2=1, A_3=0$	--
0101	1,0	--	--
0110	1,0	--	--
0111	1,0	--	--
1000	1,0	$A_2=0, A_3=1$	--
1001	0,0	--	--
1010	0,0	--	--
1011	0,0	--	--
1100	0,0	$A_2=1, A_3=1$	--
1101	1,0		T2
1101	1,1		T0

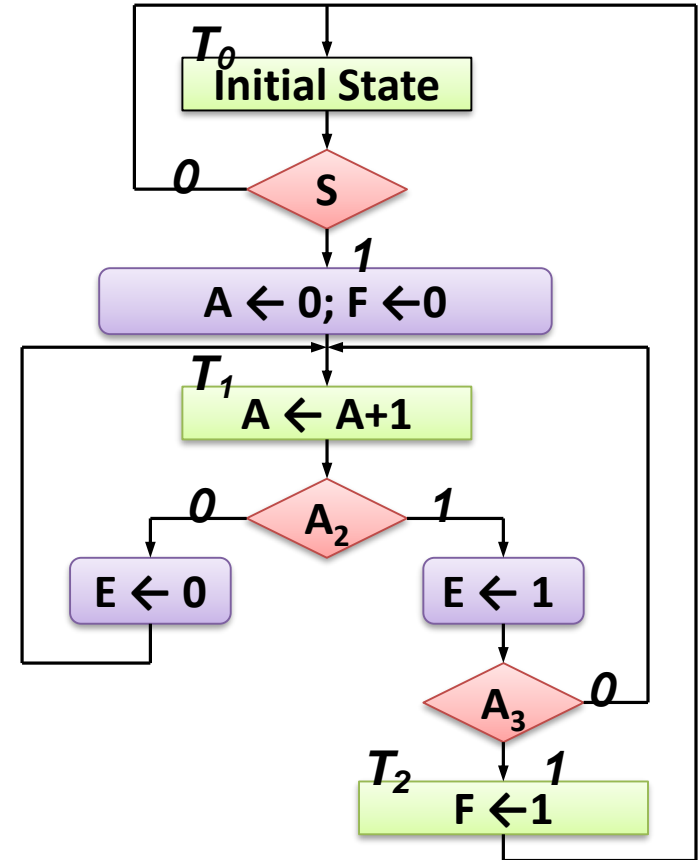

ASM Chart => Digital System

- ASM chart describes a digital system. From ASM chart, we may obtain:
 - Controller logic (via State Table/Diagram)
 - Architecture/Data Processor

1. Design of controller is determined

- from the decision boxes and the required state transitions.



2. Design requirements of data processor

- can be obtained from the operations specified with the state and conditional boxes.

ASM Chart to Controller

- Procedure:
 - Step 1: Identify all states and assign suitable codes.
 - Step 2: Formulate state table using
 - State** from state boxes
 - Inputs** from decision boxes
 - Outputs** from operations of state/conditional boxes.
 - Step 3: Obtain state/output equations and draw circuit

ASM Chart to Controller

 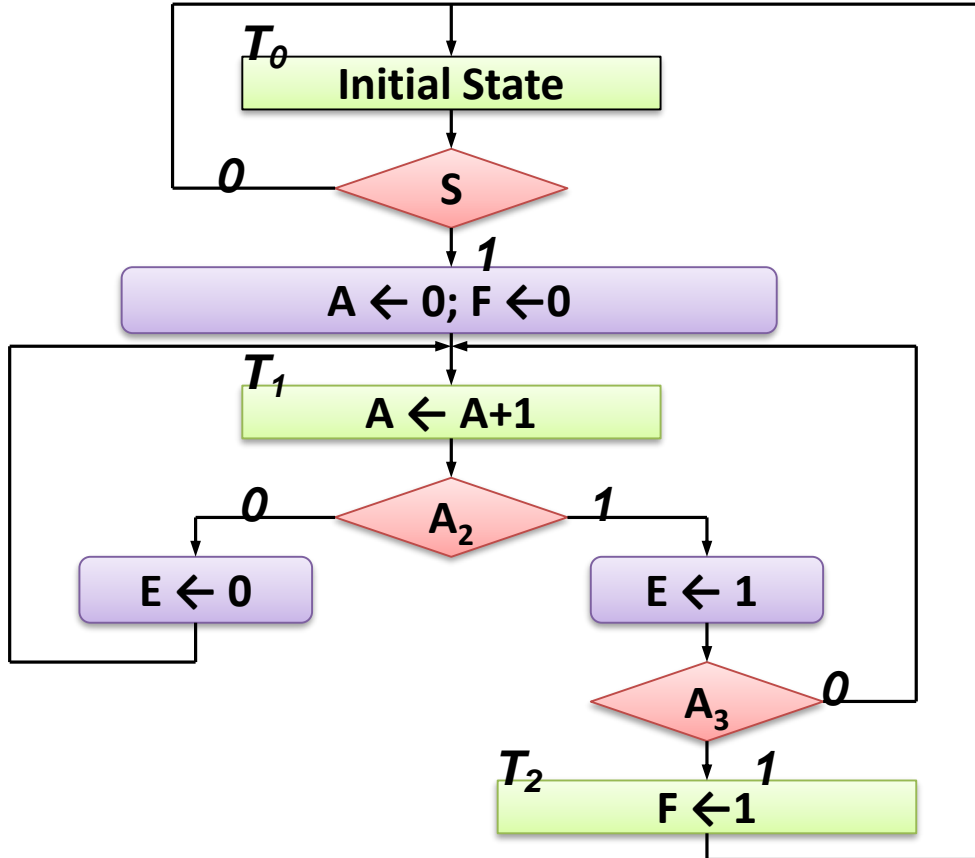

Assign codes to states:

$T_0 = 00$

$T_1 = 01$

$T_2 = 11$

Present state		inputs			Next state		outputs		
G_1	G_0	S	A_2	A_3	G_1^+	G_0^+	T_0	T_1	T_2
0	0	0	X	X	0	0	1	0	0
0	0	1	X	X	0	1	1	0	0
0	1	X	0	X	0	1	0	1	0
0	1	X	1	0	0	1	0	1	0
0	1	X	1	1	1	1	0	1	0
1	1	X	X	X	0	0	0	0	1

Inputs from conditions in decision boxes.
Outputs = present state of controller.

ASM Chart to Architecture/Data Processor

- Architecture is more difficult to design than controller.
- Nevertheless, it can be deduced from the ASM chart. In particular, the OPS from the ASM chart determine:
 - What registers to use?
 - How they can be connected?
 - What operations to support?
 - How these operations are activated?
- Guidelines:
 - Always use high-level units
 - Simplest architecture possible

ASM Chart to Architecture/Data Processor

- **Various OPS are:**

- Counter incremented ($A \leftarrow A + 1$) when state = T_1 .
- Counter cleared ($A \leftarrow 0$) when state = T_0 and $S = 1$.
- E is set ($E \leftarrow 1$) when state = T_1 and $A_2 = 1$.
- E is cleared ($E \leftarrow 0$) when state = T_1 and $A_2 = 0$.
- F is set ($F \leftarrow 0$) when state = T_2 .
- F is cleared ($F \leftarrow 0$) when state = T_0 and $S = 1$.

- **Deduce Data Path:**


- One 4-bit register A (e.g.: 4-bit synchronous counter with clear/increment).
- Two flip-flops needed for E and F (e.g.: JK/D flip-flops).

ASM Chart => Architecture/Data Processor

$F \leftarrow 0; A \leftarrow 0$
@ T_0 and $S = 1$

$A \leftarrow A + 1$ @ T_1

$E \leftarrow 1$
@ T_1 and $A_2 = 1$

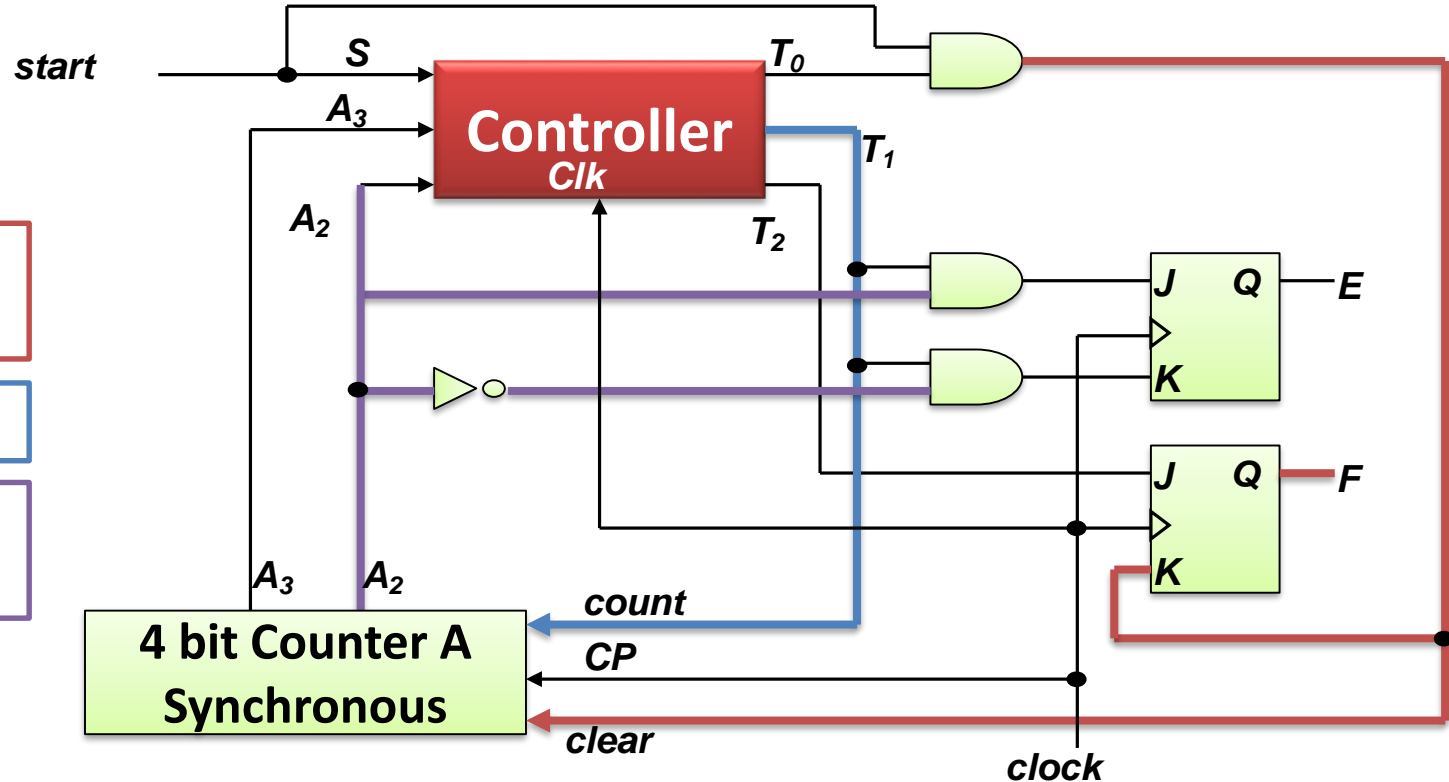

Thanks